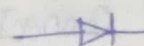
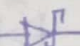


(1) Power Rectification diodes

Ex (1N4001 \rightarrow 1N4007) \rightarrow  1N4148


(2) Photo Diode

(3) Shottky Diode

Ex (1N5711, 1N5819) \rightarrow  (< 0.7)

(4) Varicap Diode

(5) Zener diode

Ex (BZX55C7V5) \rightarrow 


* ~~1N4148~~ (1N4148) \rightarrow withstand High Frequency.


\rightarrow we can check the diode by using (DMM),

in the Forward Bias \rightarrow DMM gives a value between (0.5-0.7)V.

in the backward Bias \rightarrow DMM doesn't give a value. (open loop)


* Zener diode

()

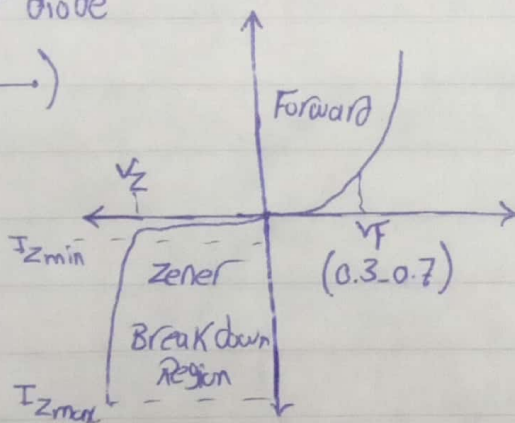

- If Current is more than I_{max} , Zener diode is damaged.

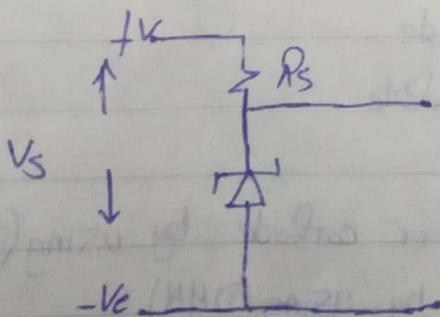- In Reverse Bias voltage will not pass if it doesn't reach (V_Z).



$R_S = \frac{V_S - V_Z}{I_Z}$, To make the current passing through Zener less than (I_{Zmax})

Examples of Zener diodes

BZX85, BZX55


13W

500mW

For Example \rightarrow BZX55C7V5

as this Zener diode its Power rating is 500mW and the Voltage output is 7.5

\rightarrow we can connect more than one Zener diode in series with each others.


*(LED diode) \rightarrow 

\rightarrow the Voltage and current of each LED varies from one to another according to the colour.

* LED Diode can be checked by using (DMM)

Applications on LED :-


\rightarrow Bi Colour LED

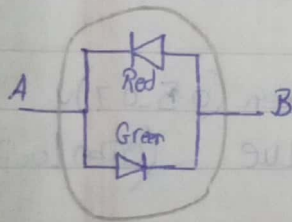


- if (A) +ve, (B) -ve \rightarrow Red LED is on and vice versa.

- if we use an AC current a Mixture colour will appear (Yellow)

\rightarrow Multi Colour LED

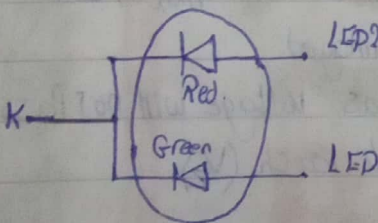

\rightarrow Seven Segment

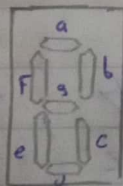


\rightarrow 1) Common anode

\rightarrow 2) Common cathode





we can determine if Seven segment is Common anode or cathode by using (DMM) and we can also determine (a, b, c, d, e, f, g) by using (DMM)

→ Dot Matrix

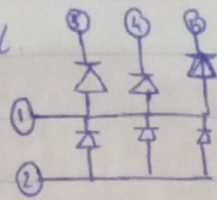

* each row and column has a common anode and cathode.

Transistors

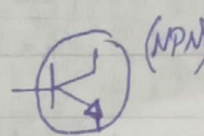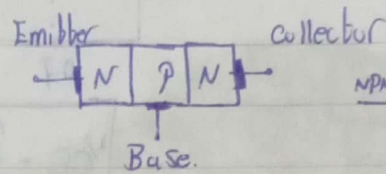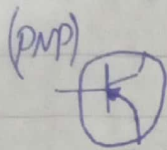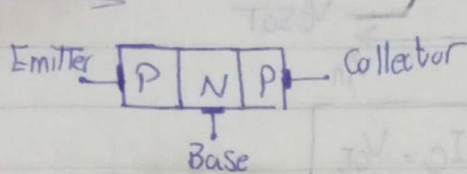

NPV → Most Common



* Current Passes From collector to the emitter, and the base control the current passing through the emitter

* we can consider the transistor as variable Resistance and the value of this Resistance varies according to the current of (I_b) base.

* As I_b inc, I_c inc.

* ~~transistor~~ ^{base} needs at least 0.7 volt greater than Emitter.

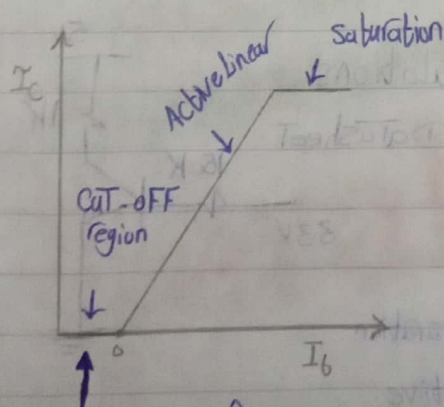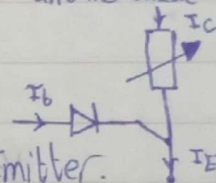* one of Advantages of Transistor that (I_b) is very small compared to (I_c) so, it permits very small current to control large currents.





in saturation region, Transistor act as a closed switch $I_b = \text{large}$

in the cut off region the Transistor act as an open switch ($I_b = 0$)

$$I_c = \beta I_b$$

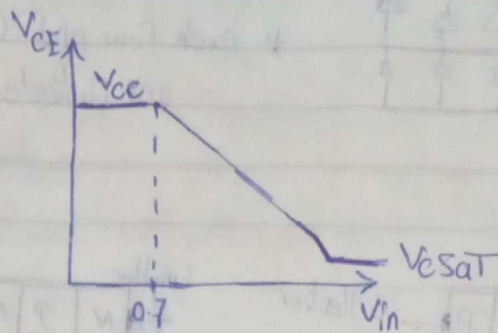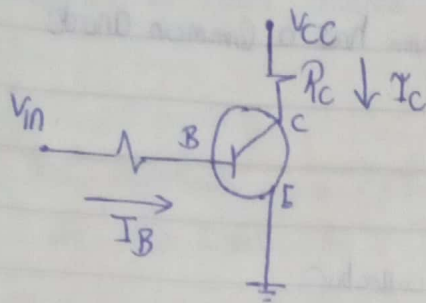* NPN Transistor is opposite to PNP Transistors



$$V_{CC} - R_C I_C = V_{CE}$$

$$\beta I_B = I_C$$

* Power dissipated by Transistors

* Determining the case of Transistor (Cut-off, Active, Saturation)


$I_B \leq 0$
Cut-off
 $I_C = 0$

$I_B > 0$
 $V_{CE} \leq 0.2V$ Saturation
 $I_C = I_{C(sat)}$

$V_{CE} > 0.2V$ Active
 $I_C = \beta I_B$

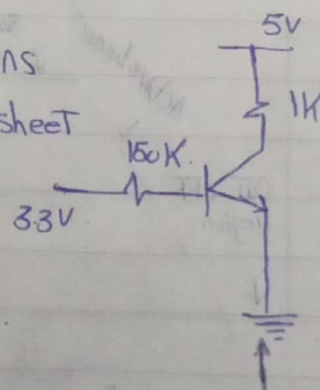Example on Transistor Circuits Calculations

$V_{BE} = 0.7V$, $\beta = 120$, $V_{CE(sat)} = 0.2V$ Datasheet



① $I_B = ?$

$$3.3 - 150 \times 10^3 I_B - 0.7 = 0$$

$$I_B = (15.3 \mu A) > 0 \begin{cases} \text{Saturation} \\ \text{Active} \end{cases}$$

② $V_{CE} = ?$

$$5V - 1K \times I_C - V_{CE} = 0$$

Assume Transistor is in an Active state, $I_C = \beta I_B = 1.84 mA$

$$\therefore V_{CE} = 3.16V > 0.2 \text{ (Active)}$$

Another Example on Determining Mode of Transistor

$$5 - 10 \times 10^3 I_B - 0.7 - 100 I_C = 0$$

Assume Transistor Active

$$I_C = \beta I_B$$

$$I_C = 120 I_B \text{ where } \beta = 120$$

$$5 - 10 \times 10^3 I_B - 0.7 - 100 \times 120 I_B = 0$$

$$I_B = 1955 \mu A \begin{matrix} \rightarrow \text{sat} \\ \rightarrow \text{Active} \end{matrix}$$



$$12 - 1 \times 10^3 I_C - V_{CE} - 100 I_C = 0$$

$$I_C = 120 \times 1955 \mu A = 23.5 \text{ mA}$$

$$\therefore V_{CE} = -13.85 < 0.2 \rightarrow \text{saturation}$$

$$\therefore 12 - 1 \times 10^3 I_C - \cancel{V_{CE}} - 100 I_C = 0$$

$$I_C = 10.73 \text{ mA} \quad \#$$

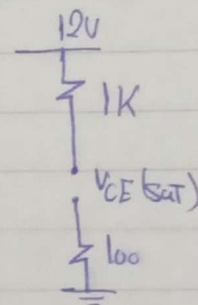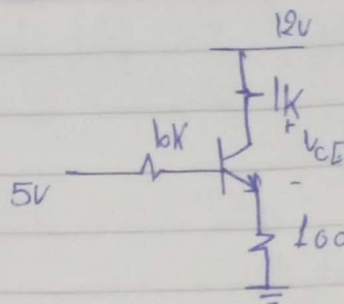

Some Examples on Common Transistors (BC547, BC337, 2N2222, BDT39, ...)

* in case of using Transistor as a switch, I_B should be more than ~~original~~ its value by 5 or 10 times.

$$R_B = \frac{V_{in} - V_{BE}}{I_B} = \frac{3.3 - 0.7}{0.91} = 2.857 \text{ k}\Omega$$